



Power electronics lab 33517B is an universal learning platform which is very useful to understand various concepts of power electronics like VI characteristics of the power electronic devices, single phase controlled rectifiers, DC to DC choppers etc. This Lab is provided with a bread board for testing their own circuits, built in AC & DC power supplies and exhaustive learning material.

Features

- 1. Self contained & easy to operate
- 2. Functional blocks indicated on board mimic
- 3. Breadboard provided for own circuit development
- 4. In built AC/DC Power Supplies
- 5. Onboard pulse generator with frequency and duty cycle control.
- 6. On board single phase controlled rectifier firing circuit
- 7. On board thyristor devices
- 8. On board pulse amplifier and isolation transformer
- 9. On board variable load and circuit components

Object

- 01. VI characteristics of power devices
- 02. Study of Single Phase Thyristor Firing Scheme
- 03. Single Phase Controlled Rectifiers
- 04. DC to DC Chopper
- 05. Single Phase Inverter
- 06. Own circuit Development
- 07. Optional circuit components for breadboard related experiments

Optional modules

Study of:

- 01. V-I characteristics of SCR
- 02. V-I characteristics of UJT
- 03. V-I characteristics of MOSFET
- 04. V-I characteristics of IGBT
- 05. V-I characteristics of DIAC
- 06. V-I characteristics of TRIAC
- 07. V-I characteristics of PUT
- 08. SCR triggered by 74121IC
- 09. SCR triggered by Op-Amp 741IC
- 10. UJT relaxation oscillator
- 11. R, RC (half wave & full wave) triggering circuit
- 12. SCR triggered by UJT

Note: Specifications are subject to change.

₹ Tesca Technologies Pvt. Ltd.S IT-2013, Ramchandrapura Industrial Area, Sitapura Extension,

Near Bombay Hospital, Vidhani Circle, Jaipur-302022, Rajasthan, India,

Tel: +91-9829132777; Email: info@tesca.in, tesca.technologies@gmail.com

∾ Website: www.tescaglobal.com



- 13. SCR triggered by 555IC
- 14. SCR triggered by PUT
- 15. SCR triggered by 74121IC
- 16. SCR triggered by Op-Amp 741IC
- 17. Lamp flasher using SCR
- 18. SCR alarm circuit

Technical Specifications

Size of Breadboard $172.5 \, \text{mm} \times 128.5 \, \text{mm}$ DC Power Supply +5 V, -5 V 500 mA, +12V, -12 V 500 mA +15 V, 250 mA

+35V, -35V, 250 mA

AC Power Supply 18V-0V-18V

0V-15V

On board Firing Circuits 30Hz to 900Hz variable

Frequency range Amplitude 12V

PWM control of G1, G2, G3 and G4

Duty cycle control of "Gate"

Signal is 0 to 100%

SCR Assembly 4 SCRs 2P4M, 400V/2A

Power Devices IGBT-G4BC20S, MOSFETIRFZ44N,

> UJT-2N2646, DIACDB3, TRIAC-BT136, PUT-

2N6027

2 nos. PT4502 1:1 and one is Pulse transformer on board

PT4503 1:1:1

Circuit Components on board : Electrolytic Capacitor 1uF, 63V

Metalized Capacitor 0.1uF, 63V Metalized Capacitor 0.33uF, 63V Diode 1N4007, Inductor 68mH, Inductor 68mH, Inductor 10mH 6 load resistances- 47E/7W,

Load selector

120E/5W, 270E/5W, 2K2/2W,

1K/1W, 1K/10W

Test points 10 nos

Power Supply (Mains) 220V/110V, 50Hz/60Hz

Included Accessories:

Bread boards 2 nos. Connecting wires 20 nos. 2mm to 1mm Patch cords 15 nos. 2mm Patch cords (Red) 16" 4 nos. 2mm Patch cords (Black)16" 4 nos. 2mm Patch cords (Blue) 16" 12 nos. Mains cord 1 no.

Optional:

- 1. Simtel Power Electronics Software
- 2. Digital Multimeter

Note: Specifications are subject to change.

₹ Tesca Technologies Pvt. Ltd.S IT-2013, Ramchandrapura Industrial Area, Sitapura Extension, Near Bombay Hospital, Vidhani Circle, Jaipur-302022, Rajasthan, India, Tel: +91-9829132777; Email: info@tesca.in, tesca.technologies@gmail.com ∾ Website: www.tescaglobal.com